


# Circuit Devices

With your current and your potential difference measured, you can now make some **sweet** graphs...

## Three Important Current-Potential Difference Graphs

$I$ - $V$  graphs show how the **current** varies as you **change** the **potential difference** (p.d.). Here are three examples, plotted from the experiment on the previous page:


### RESISTORS AND WIRES

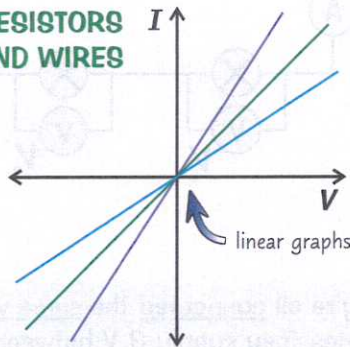

Current is **directly proportional to p.d.** (if the temperature stays the same).


Different resistors have different resistances, so their  $I$ - $V$  graphs have different **slopes**.

### FILAMENT LAMP

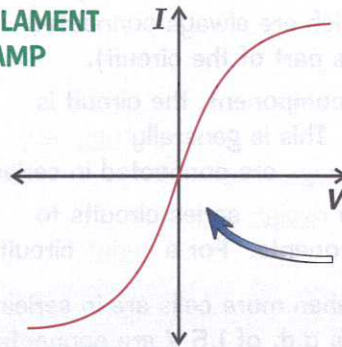

The increasing current increases the **temperature** of the filament, which makes the **resistance increase** (see p.185) so their  $I$ - $V$  graphs are **curved**.

### DIODE


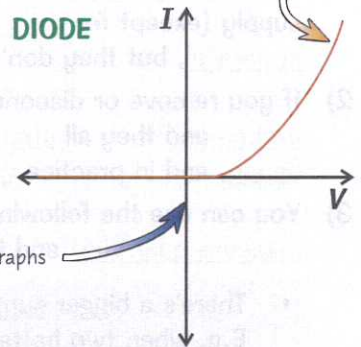


Current will only flow through a diode **in one direction**, as shown. The diode has very **high resistance** in the opposite direction.

- 1) **Linear** components have an  $I$ - $V$  graph that's a **straight line** (e.g. a fixed resistor). **Non-linear** components have a **curved**  $I$ - $V$  graph (e.g. a filament lamp or a diode).
- 2) For **linear** components, if the line goes through **(0,0)**, the resistance of the component equals the **inverse** of the **gradient** of the line, or "**1/gradient**". The **steeper** the graph, the **lower** the resistance.
- 3) You can find the **resistance** for **any point** on any  $I$ - $V$  graph by reading the **p.d.** and **current** at that point and sticking them into  $V = IR$ , p.185.



## LDR is Short for Light Dependent Resistor

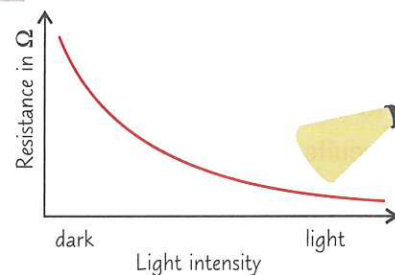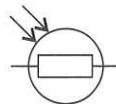- 1) An LDR is a resistor that is **dependent** on the **intensity of light**. Simple really.
- 2) In **bright light**, the resistance **falls**.
- 3) In **darkness**, the resistance is **highest**.
- 4) They have lots of applications including **automatic night lights**, outdoor lighting and **burglar detectors**.



## The Resistance of a Thermistor Decreases as Temperature Increases

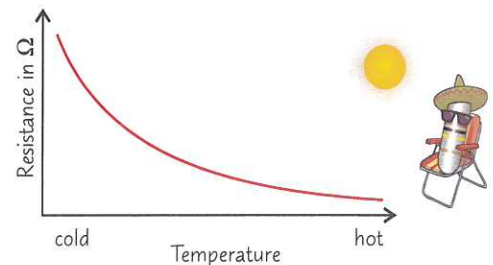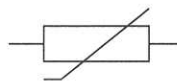- 1) A **thermistor** is a **temperature dependent** resistor.
- 2) In **hot** conditions, the resistance **drops**.
- 3) In **cool** conditions, the resistance goes **up**.
- 4) Thermistors make useful **temperature detectors**, e.g. **car engine** temperature sensors and electronic **thermostats**.



## LDRs — Light Dependent Rabbits...

You may get given an  $I$ - $V$  graph in your exam that you haven't seen before. Make sure you understand why these graphs have the shape they do, and you'll be ready for anything they throw at you.

Q1 Describe one everyday use for: a) an LDR


b) a thermistor

[2 marks]


# Circuit Devices
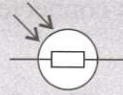
## Warm-Up


Draw lines to match each circuit symbol to the name of the component that it's representing.



thermistor

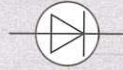

LDR

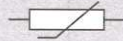

diode

1 The resistance of a thermistor changes depending on its surroundings.



a) State what happens to the resistance of a thermistor as the surrounding temperature increases.

..... [1]

b) Give **one** example of a device that uses a thermistor.


..... [1]

[Total 2 marks]


2 Filament bulbs are a common circuit component.



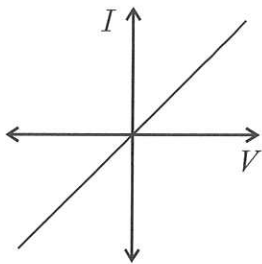
a) Which is the correct  $I$ - $V$  graph for a filament bulb?




A

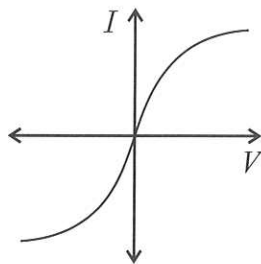

B

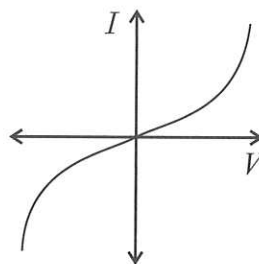

C

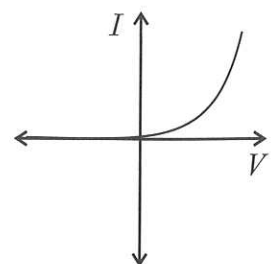

D

[1]

b) Explain why the  $I$ - $V$  graph for a filament bulb has this shape.

.....  
 .....  
 .....

[2]

[Total 3 marks]

### Exam Practice Tip

You'll need to know the  $I$ - $V$  graphs for resistors, wires and diodes too, and whether they're linear or non-linear graphs. Plus, you'll need to be able to explain how the gradient of an  $I$ - $V$  graph relates to the resistance of the component.

